Ethan Bruley

ENCE 2101

Lab 8

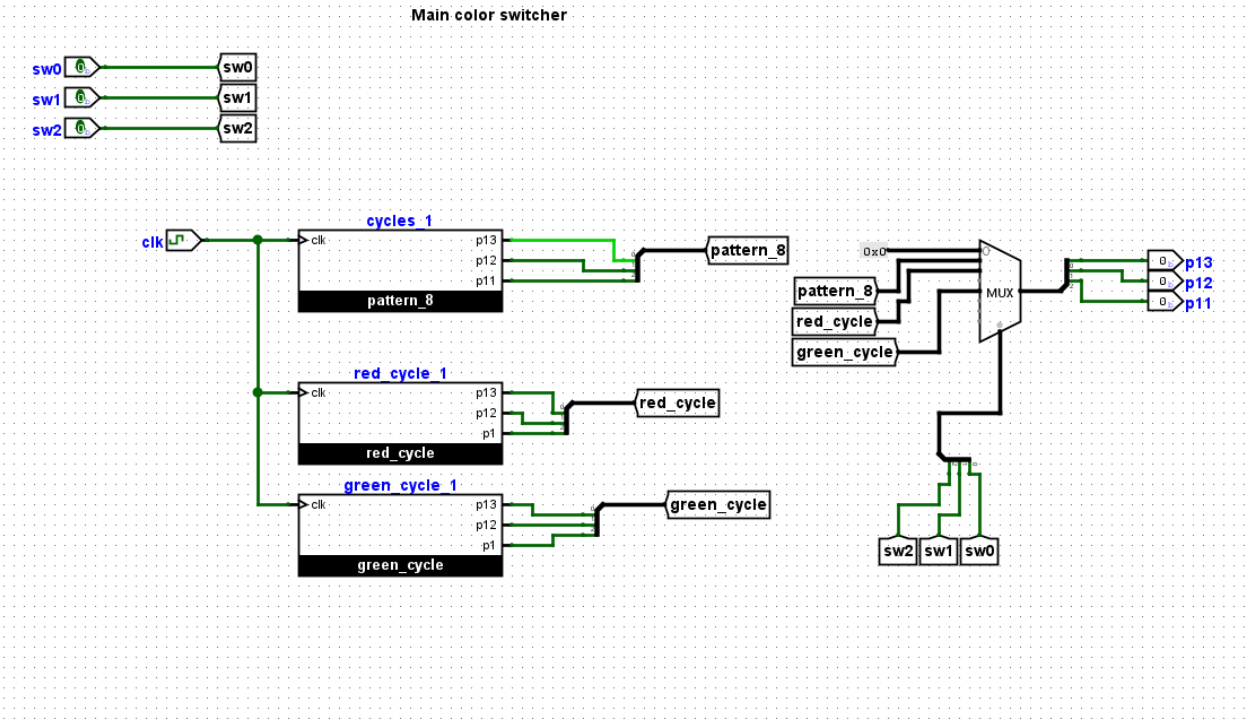


Figure 1: Main color switcher

Main circuit that utilizes 3 switches and a mux to perpetuate 4 states; lights off, 8 pattern cycle, red cycle, and green cycle. This all runs at 1 hz and uses different size muxes to change how long the lights are on and or off.

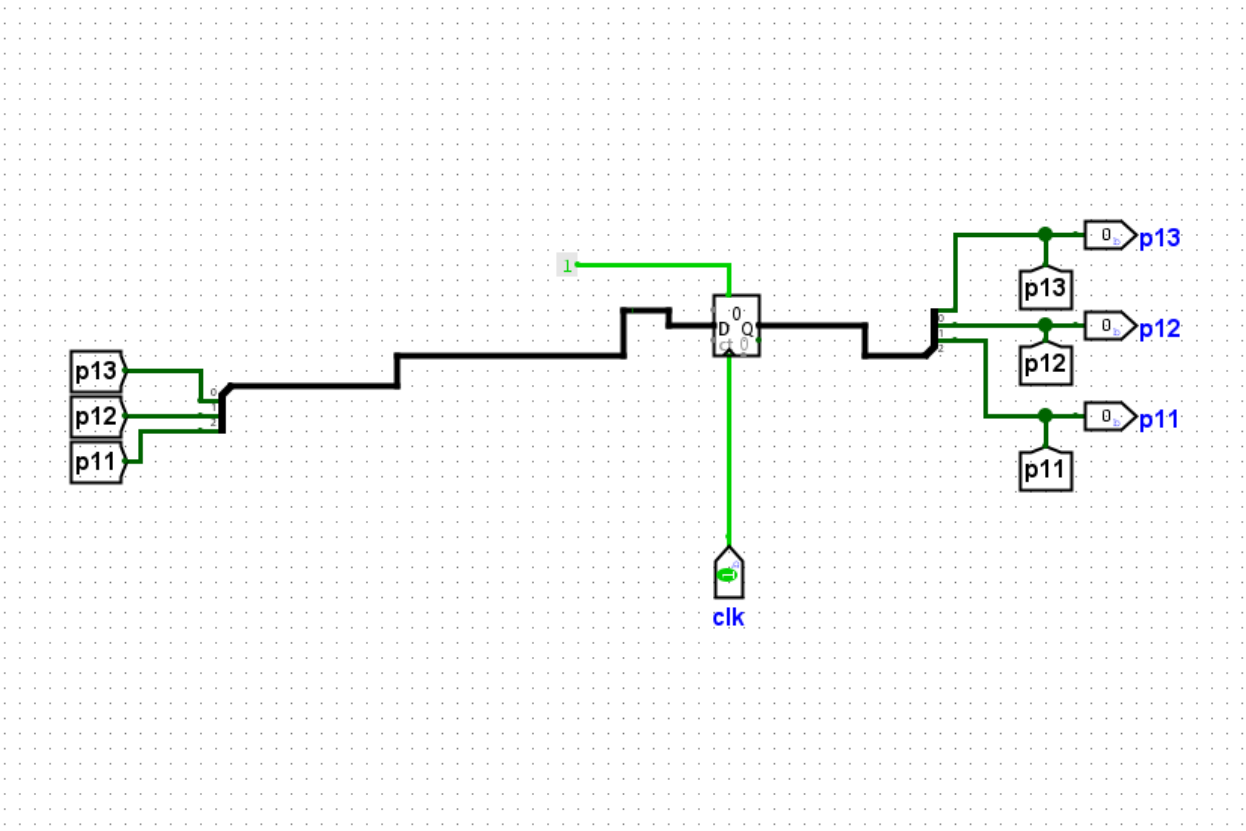


Figure 2: 8 Pattern switcher

This is the 8-pattern cycle that changes the inputs of the led based on a counter moving at 1 hz.

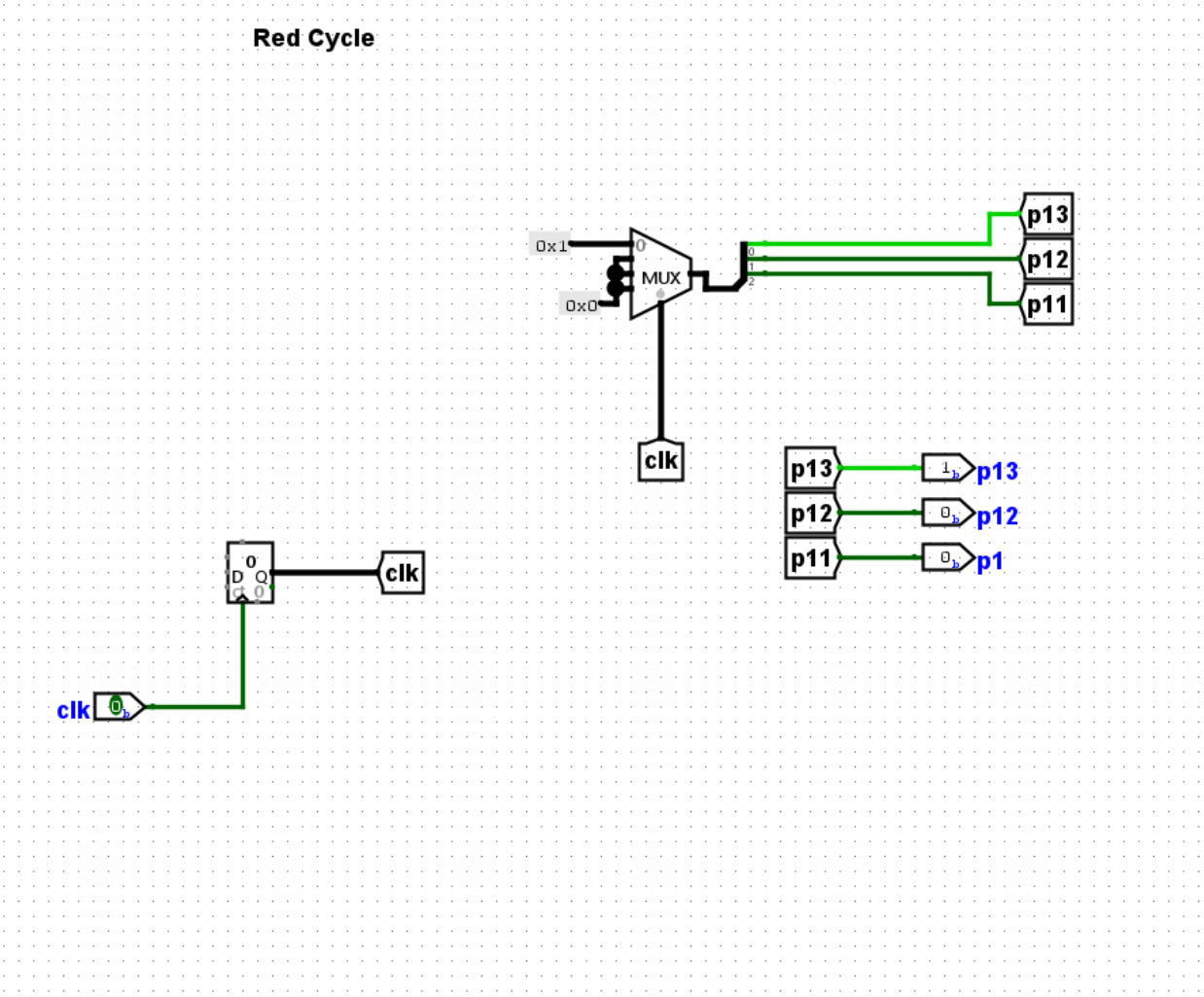


Figure 3: Red Cycle

This is the red cycle circuit that cycles red and off at 1 hz and a 4 input mux.

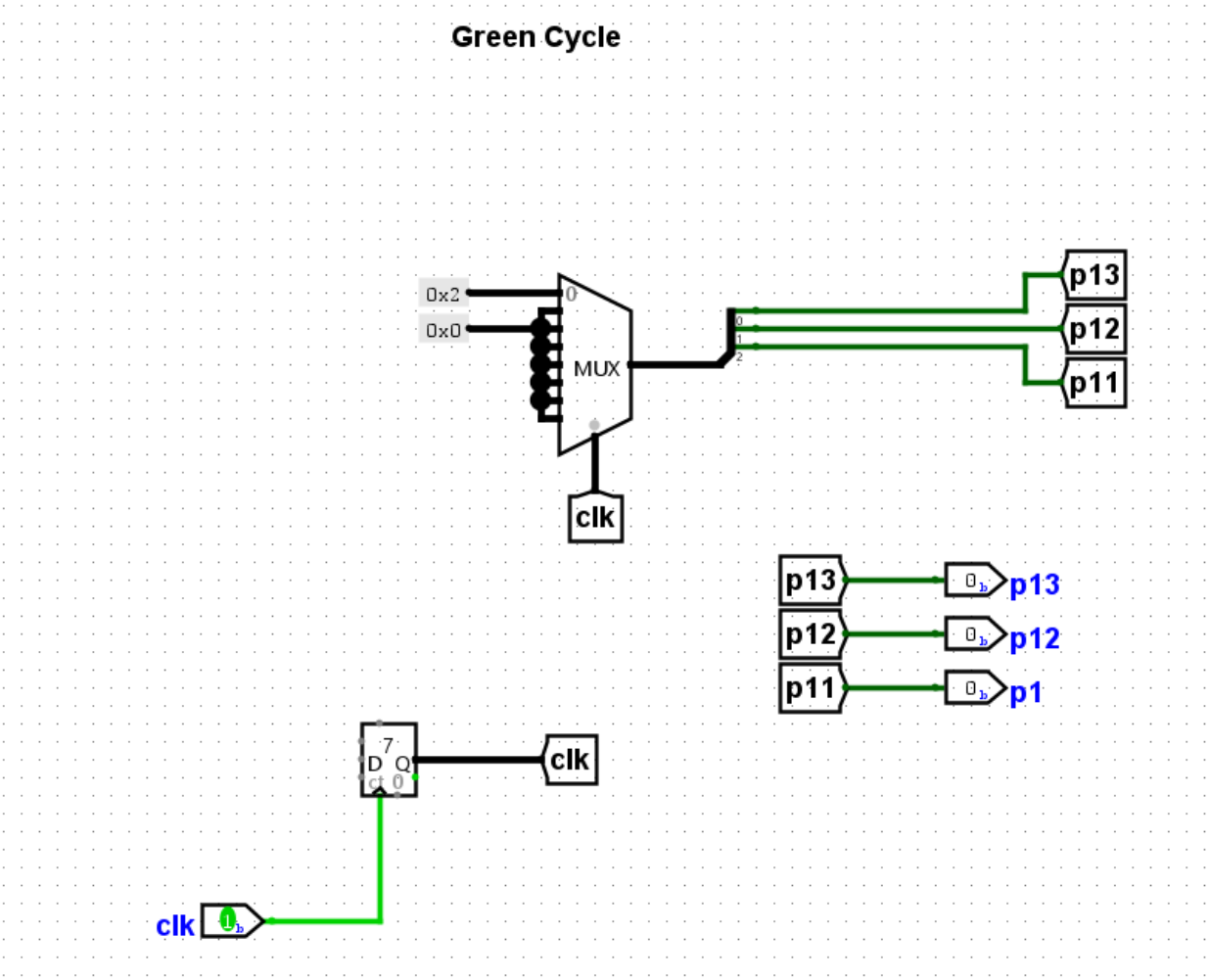


Figure 4: Green Cycle

This is the green cycle circuit that cycles red and off at 1 hz and a 4 input mux.